

Brac University
Semester: Spring 2026
Course Code: CSE250
Circuits and Electronics
Section: 01
Faculty: SDS

Name:

Set
A


- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 question(s)** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

DO NOT WRITE ANYTHING ELSE INSIDE THIS BORDER

Student ID	Answers (Q1-Q10)	Answers (Q11-Q20)	Answers (Q21-Q30)
0	A B C D	A B C D	A B C D
1	1	11	21
2	2	12	22
3	3	13	23
4	4	14	24
5	5	15	25
6			
7	A B C D	A B C D	A B C D
8	6	16	26
9	7	17	27
	8	18	28
Set Identifier	9	19	29
5	10	20	30

DO NOT WRITE ANYTHING ELSE INSIDE THIS BORDER


◇ Question 1 of 4 [CO1] [1 mark]

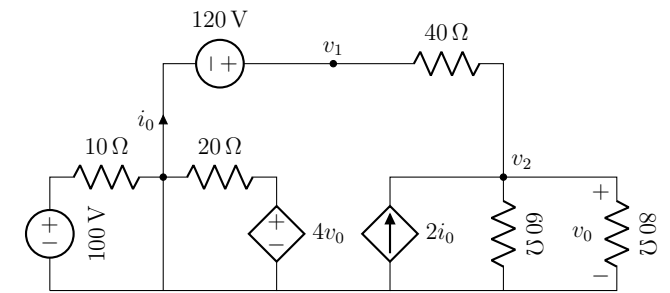

How many nodes are in this circuit?

- (a) 5 (b) 3 (c) 4 (d) 7 (e) 6


◇ Question 2 of 4 [CO3] [2 marks]

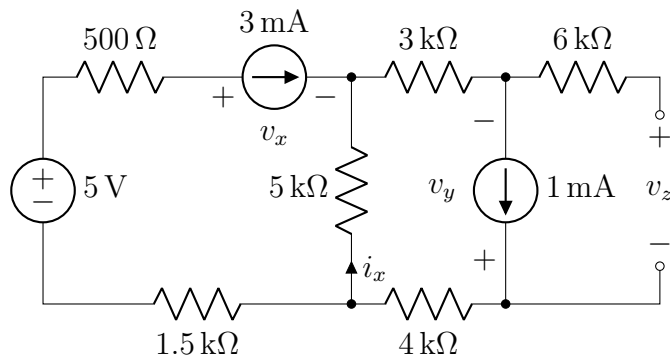

- (a) c

- (b) b
(c) a

◇ Question 3 of 4 [CO3] [5 marks]

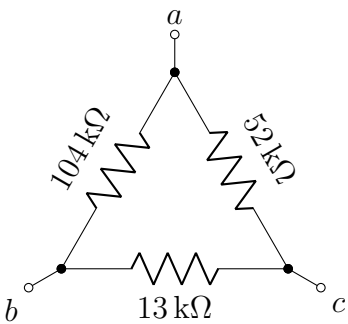

Which of the following statements is true?

(a) $R_{ab} = 40\text{ k}\Omega$, $R_{bc} = 12\text{ k}\Omega$, $R_{ca} = 36\text{ k}\Omega$

(b) $R_{ab} = R_{bc} = R_{ca} = 9.455\text{ k}\Omega$


(c) $R_{ab} = 40\text{ }\Omega$, $R_{bc} = 12\text{ }\Omega$, $R_{ca} = 36\text{ }\Omega$

(d) $R_{ab} = 104\text{ k}\Omega$, $R_{bc} = 13\text{ k}\Omega$, $R_{ca} = 52\text{ k}\Omega$

(e) None of the above

Which of the following circuits is/are impossible (violates Kirchhoff’s laws)?

◇ Question 4 of 4 [CO1] [2 marks]

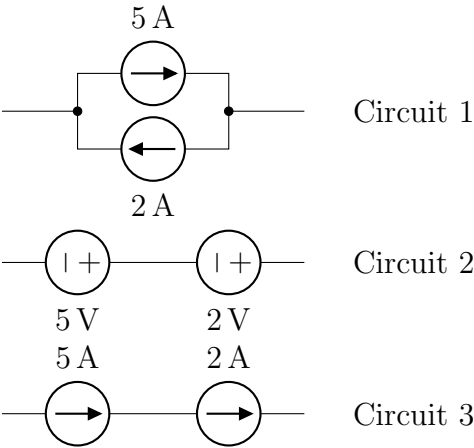

- (a) Circuit 2

(d) Circuit 3
- (b) Circuit 1 & 3

(e) None of the above
- (c) Circuit 1

Do you have any suggestion that may improve this course?

Your Suggestions

..... ↓ Your answers/roughs start here ↓



Assessment: *Main Template*
Duration: 30 minutes
Date: May 4, 2026
Full Marks: 10

Brac University
Semester: Spring 2026
Course Code: CSE250
Circuits and Electronics
Section: 01
Faculty: SDS

Set
B

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 question(s)** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

DO NOT WRITE ANYTHING ELSE INSIDE THIS BORDER

Student ID	Answers (Q1-Q10)	Answers (Q11-Q20)	Answers (Q21-Q30)
0	1 A B C D	11 A B C D	21 A B C D
1	2	12	22
2	3	13	23
3	4	14	24
4	5	15	25
5			
6			
7	6 A B C D	16 A B C D	26 A B C D
8	7	17	27
9	8	18	28
	9	19	29
	10	20	30

DO NOT WRITE ANYTHING ELSE INSIDE THIS BORDER

◇ Question 1 of 4

[CO3] [5 marks]

Which of the following statements is true?

- (a) $R_{ab} = R_{bc} = R_{ca} = 12.522\text{ k}\Omega$
- (b) $R_{ab} = 63\text{ k}\Omega$, $R_{bc} = 15\text{ k}\Omega$, $R_{ca} = 60\text{ k}\Omega$
- (c) $R_{ab} = 63\text{ }\Omega$, $R_{bc} = 15\text{ }\Omega$, $R_{ca} = 60\text{ }\Omega$
- (d) $R_{ab} = 144\text{ k}\Omega$, $R_{bc} = 16\text{ k}\Omega$, $R_{ca} = 96\text{ k}\Omega$
- (e) None of the above

◇ Question 2 of 4


[CO3] [2 marks]

Which of the following is correct?

- (a) c
- (b) b
- (c) a

◇ Question 3 of 4

[CO1] [1 mark]

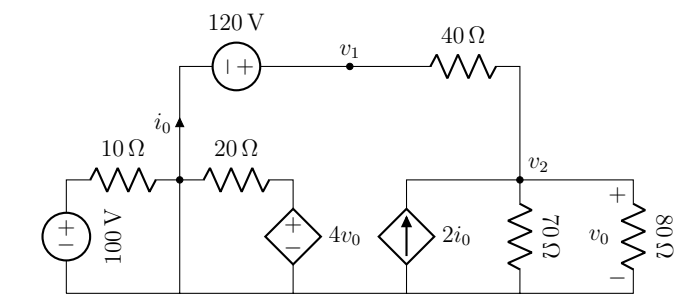


How many nodes are in this circuit?

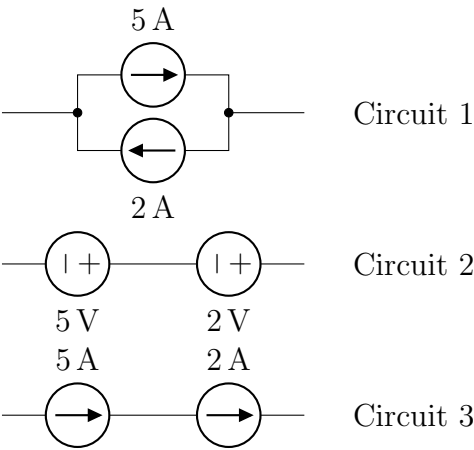- (a) 6 (b) 4 (c) 3 (d) 5 (e) 7

◆ Question 4 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff’s laws)?



- (a) Circuit 3 (b) Circuit 1 (c) Circuit 1 & 3
(d) Circuit 2 (e) None of the above
- Do you have any suggestion that may improve this course?

Your Suggestions

..... ↓ Your answers/roughs start here ↓

Name:



Brac University

Semester: Spring 2026
Course Code: CSE250
Circuits and Electronics
Section: 01
Faculty: SDS

Set
C

Assessment: *Main Template*
Duration: 30 minutes
Date: May 4, 2026
Full Marks: 10


- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 question(s)** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

DO NOT WRITE ANYTHING ELSE INSIDE THIS BORDER

Student ID	Answers (Q1-Q10)	Answers (Q11-Q20)	Answers (Q21-Q30)
0	A B C D	A B C D	A B C D
1	1	11	21
2	2	12	22
3	3	13	23
4	4	14	24
5	5	15	25
6			
7	A B C D	A B C D	A B C D
8	6	16	26
9	7	17	27
	8	18	28
Set Identifier	9	19	29
5	10	20	30


DO NOT WRITE ANYTHING ELSE INSIDE THIS BORDER

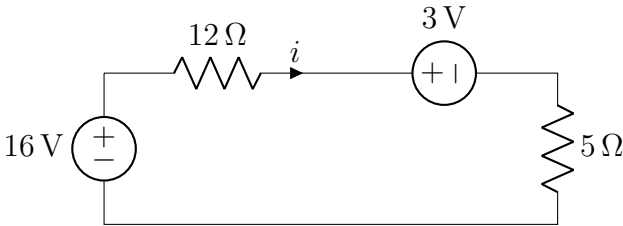◇ Question 1 of 4 [CO3] [2 marks] What’s the relation between v_1, v_2 and i ?



- (a) $-16 + 12i - 3 + 5i = 0$
- (b) $-16 - 12i - 3 + 5i = 0$
- (c) $-16 - 12i + 3 + 5i = 0$
- (d) $-16 + 12i + 3 + 5i = 0$
- (e) None of the above


◇ Question 2 of 4 [CO3] [5 marks]

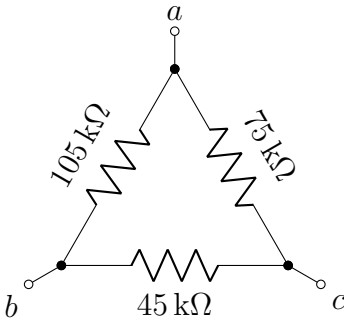

Which of the following statements is true?

- (a) $R_{ab} = R_{bc} = R_{ca} = 22.183\text{ k}\Omega$
- (b) $R_{ab} = 56\text{ }\Omega, R_{bc} = 36\text{ }\Omega, R_{ca} = 50\text{ }\Omega$
- (c) $R_{ab} = 105\text{ k}\Omega, R_{bc} = 45\text{ k}\Omega, R_{ca} = 75\text{ k}\Omega$
- (d) $R_{ab} = 56\text{ k}\Omega, R_{bc} = 36\text{ k}\Omega, R_{ca} = 50\text{ k}\Omega$
- (e) None of the above

◆ Question 3 of 4 [CO1] [1 mark]

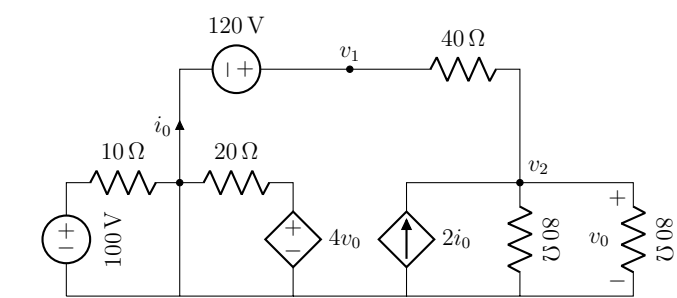


How many nodes are in this circuit?

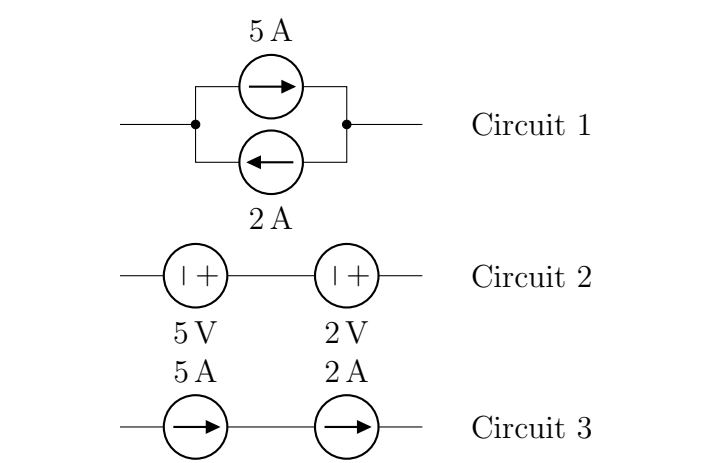- (a) 7
- (b) 5
- (c) 3
- (d) 4
- (e) 6

◆ Question 4 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff’s laws)?



- (a) Circuit 1
- (b) Circuit 1 & 3
- (c) Circuit 2
- (d) Circuit 3
- (e) None of the above
- Do you have any suggestion that may improve this course?

Your Suggestions

..... ↓ Your answers/roughs start here ↓

Name:



Brac University

Semester: Spring 2026

Course Code: CSE250

Circuits and Electronics

Section: 01

Faculty: SDS

Set
D

Assessment: *Main Template*

Duration: 30 minutes

Date: May 4, 2026

Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 question(s)** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.


DO NOT WRITE ANYTHING ELSE INSIDE THIS BORDER

Student ID	Answers (Q1-Q10)	Answers (Q11-Q20)	Answers (Q21-Q30)
0	A B C D	A B C D	A B C D
1	1	11	21
2	2	12	22
3	3	13	23
4	4	14	24
5	5	15	25
6			
7	A B C D	A B C D	A B C D
8	6	16	26
9	7	17	27
	8	18	28
Set Identifier	9	19	29
5	10	20	30

DO NOT WRITE ANYTHING ELSE INSIDE THIS BORDER


◇ Question 1 of 4 [CO1] [2 marks]

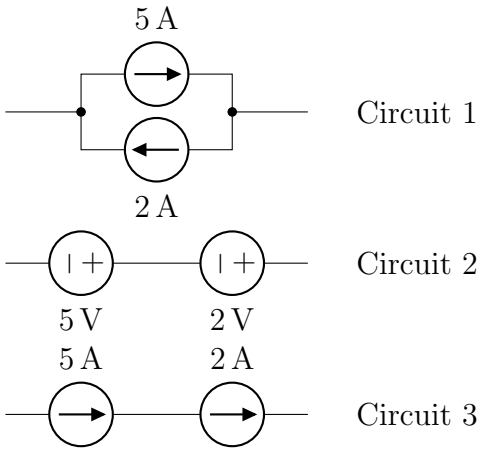Which of the following circuits is/are impossible (violates Kirchhoff’s laws)?



- (a) Circuit 1 & 3 (b) Circuit 2 (c) Circuit 1
(d) Circuit 3 (e) None of the above


◇ Question 2 of 4 [CO3] [2 marks]

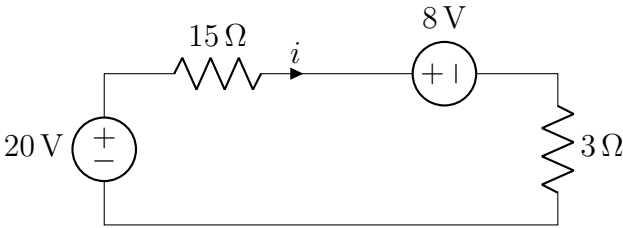

What's the relation between v_1, v_2 and i ?

- (a) $-20 + 15i + 8 + 3i = 0$
- (b) $-20 - 15i - 8 + 3i = 0$
- (c) $-20 + 15i - 8 + 3i = 0$
- (d) $-20 - 15i + 8 + 3i = 0$
- (e) None of the above


◇ Question 3 of 4 [CO1] [1 mark]

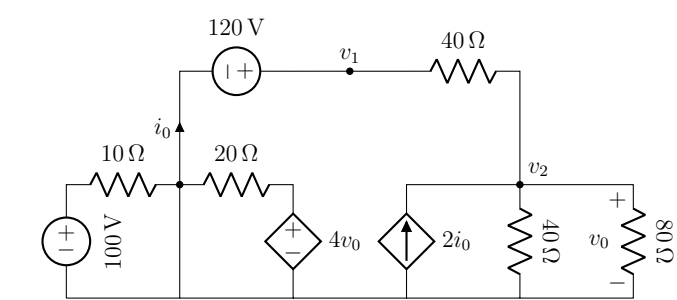

How many nodes are in this circuit?

- (a) 6
- (b) 5
- (c) 3
- (d) 7
- (e) 4

◇ Question 4 of 4 [CO3] [5 marks]

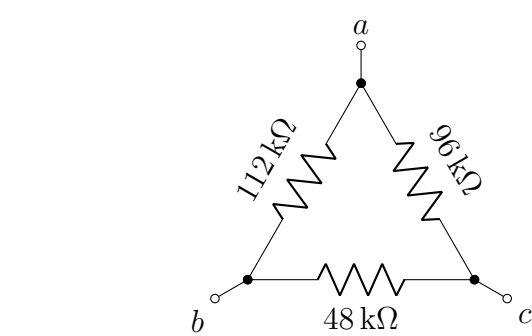

Which of the following statements is true?

- (a) $R_{ab} = R_{bc} = R_{ca} = 24.889\text{ k}\Omega$
- (b) $R_{ab} = 63\text{ k}\Omega, R_{bc} = 39\text{ k}\Omega, R_{ca} = 60\text{ k}\Omega$
- (c) $R_{ab} = 63\text{ }\Omega, R_{bc} = 39\text{ }\Omega, R_{ca} = 60\text{ }\Omega$
- (d) $R_{ab} = 112\text{ k}\Omega, R_{bc} = 48\text{ k}\Omega, R_{ca} = 96\text{ k}\Omega$
- (e) None of the above

Do you have any suggestion that may improve this course?

Your Suggestions

..... ↓ Your answers/roughs start here ↓

